
Fundamentals of Logic Design Enhanced Edition 7th edition Roth Solutions Manual

SKU: 9781337620352-SOLUTIONS


Unit 2 Problem Solutions

2.1 *See FLD p. 731 for solution.*

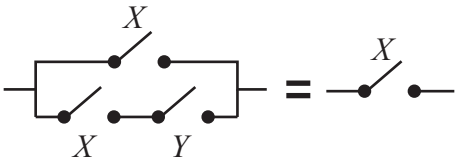2.2 (a) In both cases, if X = 0, the transmission is 0, and if X = 1, the transmission is 1.



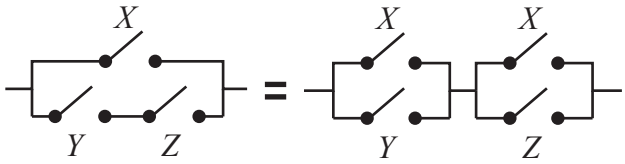2.2 (b) In both cases, if X = 0, the transmission is YZ, and if X = 1, the transmission is 1.



2.3 *Answer is in FLD p. 731*

2.4 (a) $F = [(A \cdot 1) + (A \cdot 1)] + E + BCD = A + E + BCD$

2.4 (b) $Y = (AB' + (AB + B))\,B + A = (AB' + B)\,B + A$
$= (A + B)\,B + A = AB + B + A = A + B$

2.5 (a) $(A + B)\,(C + B)\,(D' + B)\,(ACD' + E)$
$= (AC + B)\,(D' + B)\,(ACD' + E)$ By Dist. Law
$= (ACD' + B)\,(ACD' + E)$ By Dist. Law
$= ACD' + BE$ By Dist. Law

2.5 (b) $(A' + B + C')\,(A' + C' + D)\,(B' + D')$
$= (A' + C' + BD)\,(B' + D')$
{By Distributive Law with $X = A' + C'$}
$= A'B' + B'C' + B'BD + A'D' + C'D' + BDD'$
$= A'B' + A'D' + C'B' + C'D'$

2.6 (a) $AB + C'D' = (AB + C')\,(AB + D')$
$= (A + C')\,(B + C')\,(A + D')\,(B + D')$

2.6 (b) $WX + WY'X + ZYX = X(W + WY' + ZY)$
$= X(W + ZY)$ {By Absorption}
$= X(W + Z)\,(W + Y)$

2.6 (c) $A'BC + EF + DEF' = A'BC + E(F + DF')$
$= A'BC + E(F + D) = (A'BC + E)\,(A'BC + F + D)$
$= (A' + E)\,(B + E)\,(C + E)\,(A' + F + D)$
$(B + F + D)\,(C + F + D)$


2.6 (d) $XYZ + W'Z + XQ'Z = Z(XY + W' + XQ')$
$= Z[W' + X(Y + Q')]$
$= Z(W' + X)\,(W' + Y + Q')$ By Distributive Law


2.6 (e) $ACD' + C'D' + A'C = D'\,(AC + C') + A'C$
$= D'\,(A + C') + A'C$ By Elimination Theorem
$= (D' + A'C)\,(A + C' + A'C)$
$= (D' + A')\,(D' + C)\,(A + C' + A')$
By Distributive Law and Elimination Theorem
$= (A' + D')\,(C + D')$

2.6 (f) $A + BC + DE$
$= (A + BC + D)(\,A + BC + E)$
$= (A + B + D)(A + C + D)(A + B + E)(A + C + E)$

2.7 (a) $(\underline{A + B + C} + D)\,(\underline{A + B + C} + E)\,(\underline{A + B + C} + F)$
$= \underline{A + B + C} + DEF$
Apply second Distributive Law twice

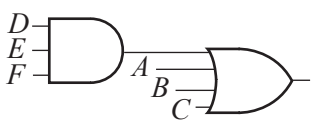2.7 (b) $W\underline{XYZ} + V\underline{XYZ} + U\underline{XYZ} = \underline{XYZ}\,(W + V + U)$
By first Distributive Law



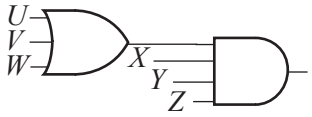

2.8 (a) $[(AB)' + C'D]' = AB(C'D)' = AB(C + D')$
$= ABC + ABD'$

2.8 (b) $[A + B\,(C' + D)]' = A'(B(C' + D))'$
$= A'(B' + (C' + D)') = A'(B' + CD')$
$= A'B' + A'CD'$

2.8 (c) $((A + B')\,C)'\,(A + B)\,(C + A)'$
$= (A'B + C')\,(A + B)C'A' = (A'B + C')A'BC'$
$= A'BC'$


2.9 (a) $F = [(A + B)' + (A + (A + B)')']\,(A + (A + B)')'$
$= (A + (A + B)')'$
By Elimination Theorem with
$X = (A + (A + B)')' = A'(A + B) = A'B$

2.9 (b) G = {[(R + S + T)' PT(R + S)']' T}'
$= (R + S + T)'\,PT(R + S)' + T'$
$= T' + (R'S'T')\,P(R'S')T = T' + PR'S'T'T = T'$


© 2021 Cengage. All Rights Reserved. May not be scanned, copied or duplicated, or posted to a publicly accessible website, in whole or in part.

Fundamentals of Logic Design Enhanced Edition 7th edition Roth Solutions Manual


2.10 (a)

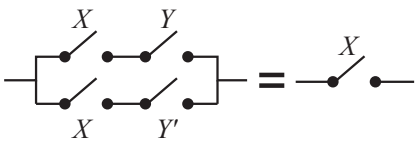


2.10 (b)

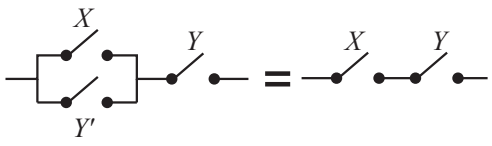


2.10 (c)

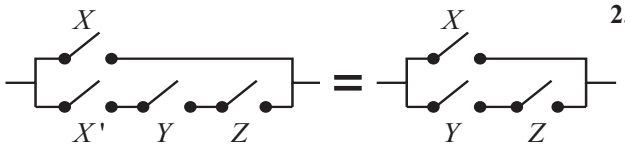


2.10 (d)

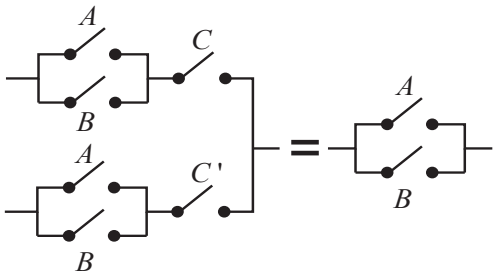

2.10 (e)

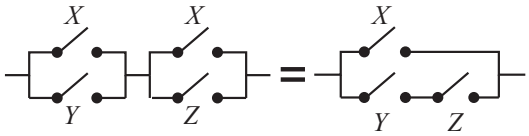

2.10 (f)

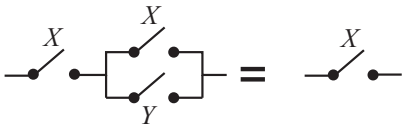

2.11 (a) $(A' + B' + C)(A' + B' + C)' = 0$ By Complementarity Law

2.11 (b) $AB(C' + D) + B(C' + D) = B(C' + D)$ By Absorption

2.11 (c) $AB + (C' + D)(AB)' = AB + C' + D$
By Elimination Theorem

2.11 (d) $(A'BF + CD')(A'BF + CEG) = A'BF + CD'EG$
By Distributive Law

2.11 (e) $[AB' + (C + D)' + E'F](C + D)$
$= AB'(C + D) + E'F(C + D)$ Distributive Law

2.11 (f) $A'(B + C)(D'E + F)' + (D'E + F)$
$= A'(B + C) + D'E + F$ By Elimination

2.12 (a) $(X + Y'Z) + (X + Y'Z)' = 1$ By Complementarity Law

2.12 (b) $[W + X'(Y + Z)][W' + X'(Y + Z)] = X'(Y + Z)$
By Uniting Theorem

2.12 (c) $(V'W + UX)'(UX + Y + Z + V'W) = (V'W + UX)'$
$(Y + Z)$ By Elimination Theorem

2.12 (d) $(UV' + W'X)(UV' + W'X + Y'Z) = UV' + W'X$
By Absorption Theorem

2.12 (e) $(W' + X)(Y + Z') + (W' + X)'(Y + Z')$
$= (Y + Z')$ By Uniting Theorem

2.12 (f) $(V' + U + W)[(W + X) + Y + UZ'] + [(W + X) + UZ' + Y] = (W + X) + UZ' + Y$ By Absorption

2.13 (a) $F_1 = A'A + B + (B + B) = 0 + B + B = B$

2.13 (b) $F_2 = A'A' + AB' = A' + AB' = A' + B'$

2.13 (c) $F_3 = [(AB + C)'D][(AB + C) + D]$
$= (AB + C)'D\,(AB + C) + (AB + C)'\,D$
$= (AB + C)'\,D$ By Absorption

2.13 (d) $Z = [(A + B)C]' + (A + B)CD = [(A + B)C]' + D$
By Elimination with $X = [(A + B)\,C]'$
$= A'B' + C' + D'$

2.14 (a) $ACF(B + E + D)$

2.14 (b) $W + Y + Z + VUX$

2.15 (a) $f' = \{[A + (BCD)']'[(AD)' + B(C' + A)]\}'$
$= [A + (BCD)']' + [(AD)' + B(C' + A)]'$
$= A'(BCD)'' + (AD)''[B(C' + A)]'$
$= A'BCD + AD[B' + (C' + A)']$
$= A'BCD + AD[B' + C''A']$
$= A'BCD + AD[B' + CA']$

2.15(b) $f' = [AB'C + (A' + B + D)(ABD' + B')]'$
$= (AB'C)'[(A' + B + D)(ABD' + B']'$
$= (A' + B'' + C')[(A' + B + D)' + (ABD')'B'']$
$= (A' + B + C')[A''B'D' + (A' + B' + D'')B]$
$= (A' + B + C')[AB'D' + (A' + B' + D)B]$

2.16 (a) $f^{\mathrm{D}} = [A + (BCD)'][(AD)' + B(C' + A)]^D$
$= [A\,(B + C + D)'] + [(A + D)'(B + C'A)]$

2.16 (b) $f^{\mathrm{D}} = [AB'C + (A' + B + D)(ABD' + B')]^{\mathrm{D}}$
$= (A + B' + C)[A'BD + (A + B + D')B')]$

2.17 (a) $f = [(A' + B')C] + [A(B + C')]$
$= A'C + B'C + AB + AC'$
$= A'C + B'C + AB + AC' + BC$
$= A'C + C + AB + AC' = C + AB + A = C + A$

2.17 (b) $f = A'C + B'C + AB + AC' = A + C$

2.17 (c) $f = (A' + B' + A)(A + C)(A' + B' + C' + B)$
$(B + C + C') = (A + C)$

2.18 (a) product term, sum-of-products, product-of-sums)

© 2021 Cengage. All Rights Reserved. May not be scanned, copied or duplicated, or posted to a publicly accessible website, in whole or in part.

Fundamentals of Logic Design Enhanced Edition 7th edition Roth Solutions Manual


2.18 (b) sum-of-products

2.18 (c) none apply

2.18 (d) sum term, sum-of-products, product-of-sums


2.18 (e) product-of-sums

2.19

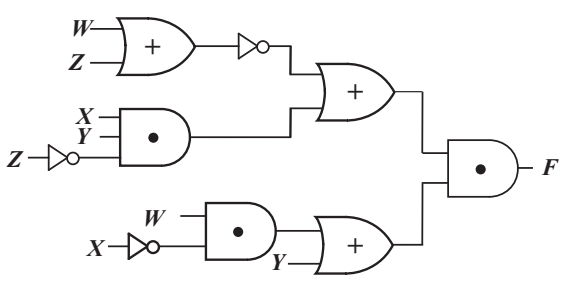


2.20 (a) $F = D[(A' + B')C + AC']$

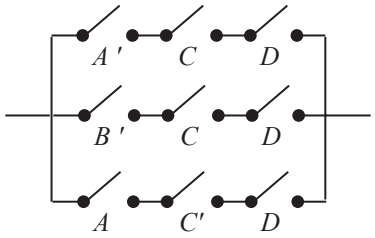2.20 (b) $F = D[(A' + B')C + AC']$
$= A'CD + B'CD + AC'D$



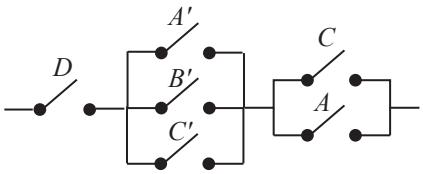2.20 (c) $F = D[(A' + B')C + AC']$
$= D(A' + B' + AC')(C + AC')$
$= D(A' + B' + C')(C + A)$



2.21

A	B	C	H	F	G
0	0	0	0	0	0
0	0	1	1	1	x
0	1	0	1	0	1
0	1	1	1	1	x
1	0	0	0	0	0
1	0	1	1	0	1
1	1	0	0	0	0
1	1	1	1	1	x

2.22 (a) $A'B' + A'CD + A'DE'$
$= A'(B' + CD + DE')$
$= A'[B' + D(C + E')]$
$= A'(B' + D)(B' + C + E')$

2.22 (b) $H'I' + JK$
$= (H'I' + J)(H'I' + K)$
$= (H' + J)(I' + J)(H' + K)(I' + K)$

2.22 (c) $A'BC + AB'C + CD'$
$= C(A'B + AB' + D')$
$= C[(A + B)(A' + B') + D']$
$= C(A + B + D')(A' + B' + D')$

2.22 (d) $A'B' + (CD' + E) = A'B' + (C + E)(D' + E)$
$= (A'B' + C + E)(A'B' + D' + E)$
$= (A' + C + E)(B' + C + E)$
$(A' + D' + E)(B' + D' + E)$

2.22 (e) $A'B'C + B'CD' + EF' = A'B'C + B'CD' + EF'$
$= B'C(A' + D') + EF'$
$= (B'C + EF')(A' + D' + EF')$
$= (B' + E)(B' + F')(C + E)(C + F')$
$(A' + D' + E)(A' + D' + F')$

2.22 (f) $WX'Y + W'X' + W'Y' = X'(WY + W') + W'Y'$
$= X'(W' + Y) + W'Y'$
$= (X' + W')(X' + Y')(W' + Y + W')(W' + Y + Y')$
$= (X' + W')(X' + Y')(W' + Y)$

2.23 (a) $W + U'YV = (W + U')(W + Y)(W + V)$

2.23 (b) $TW + UY' + V$
$= (T+U+V)(T+Y'+V)(W+U+V)(W+Y'+V)$

2.23 (c) $A'B'C + B'CD' + B'E' = B'(A'C + CD' + E')$
$= B'[E' + C(A' + D')]$
$= B'(E' + C)(E' + A' + D')$

2.23 (d) $ABC + ADE' + ABF' = A(BC + DE' + BF')$
$= A[DE' + B(C + F')]$
$= A(DE' + B)(DE' + C + F')$
$= A(B + D)(B + E')(C + F' + D)(C + F' + E')$

© 2021 Cengage. All Rights Reserved. May not be scanned, copied or duplicated, or posted to a publicly accessible website, in whole or in part.

Fundamentals of Logic Design Enhanced Edition 7th edition Roth Solutions Manual

2.24 (a) $[(XY')' + (X' + Y)'Z] = X' + Y + (X' + Y)'Z$
$= X' + Y' + Z$ By Elimination Theorem with X
$= (X' + Y)$

2.24 (b) $(X + (Y'(Z + W)')')' = X'Y'(Z + W)' = X'Y'Z'W'$

2.24 (c) $[(A' + B')' + (A'B'C)' + C'D]'$
$= (A' + B')A'B'C(C + D') = A'B'C$

2.24 (d) $(A + B)CD + (A + B)' = CD + (A + B)'$
{By Elimination Theorem with $X = (A + B)'$}
$= CD + A'B'$

2.25 (a) $F(P, Q, R, S)' = [(R' + PQ)S]' = R(P' + Q') + S'$
$= RP' + RQ' + S'$

2.25 (b) $F(W, X, Y, Z)' = [X + YZ(W + X')]'$
$= [X + X'YZ + WYZ]'$
$= [X + YZ + WYZ]' = [X + YZ]'$
$= X'Y' + X'Z'$


2.25 (c) $F(A, B, C, D)' = [A' + B' + ACD]'$
$= [A' + B' + CD]' = AB(C' + D')$

2.26 (a) $F = [(A' + B)'B]'C + B = [A' + B + B']C + B$
$= C + B$


2.26 (b) $G = [(AB)'(B + C)]'C = (AB + B'C')C = ABC$

2.26 (c) $H = [W'X'(Y' + Z')]' = W + X + YZ$

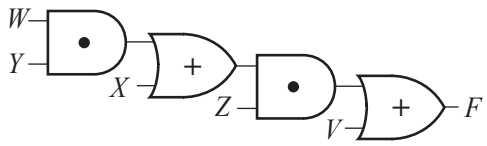2.27 $F = (\underline{V + X} + W)\ (\underline{V + X} + Y)\ (V + Z)$
$= (V + X + WY)(V + Z) = V + Z\ (X + WY)$
By Distributive Law with $X = V$




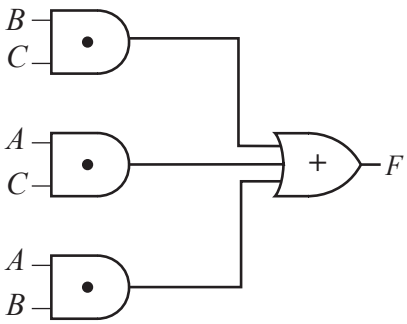2.28 (a) $F = ABC + A'BC + AB'C + ABC'$
$= BC + AB'C + ABC'$ (By Uniting Theorem)
$= C\ (B + AB') + ABC' = C\ (A + B) + ABC'$
(By Elimination Theorem)
$= AC + BC + ABC' = AC + B\ (C + AC')$
$= AC + B\ (A + C) = AC + AB + BC$



2.28 (b) Beginning with the answer to (a):

$F = A\ (B + C) + BC$

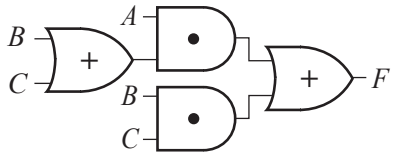

Alternate solutions:

$F = AB + C(A + B)$

$F = AC + B(A + C)$

2.29 (a)

$X\ Y\ Z$	$X+Y$	$X'+Z$	$(X+Y)$ $(X'+Z)$	XZ	$X'Y$	$XZ+X'Y$
0 0 0	0	1	0	0	0	0
0 0 1	0	1	0	0	0	0
0 1 0	1	1	1	0	1	1
0 1 1	1	1	1	0	1	1
1 0 0	1	0	0	0	0	0
1 0 1	1	1	1	1	0	1
1 1 0	1	0	0	0	0	0
1 1 1	1	1	1	1	0	1

2.29 (b)

$X\ Y\ Z$	$X+Y$	$Y+Z$	$X'+Z$	$(X+Y)$ $(Y+Z)$ $(X'+Z)$	$(X+Y)$ $(X'+Z)$
0 0 0	0	0	1	0	0
0 0 1	0	1	1	0	0
0 1 0	1	1	1	1	1
0 1 1	1	1	1	1	1
1 0 0	1	0	0	0	0
1 0 1	1	1	1	1	1
1 1 0	1	1	0	0	0
1 1 1	1	1	1	1	1

© 2021 Cengage. All Rights Reserved. May not be scanned, copied or duplicated, or posted to a publicly accessible website, in whole or in part.

Fundamentals of Logic Design Enhanced Edition 7th edition Roth Solutions Manual

2-29 (c)

X Y Z	XY	YZ	X'Z	XY+YZ+X'Z	XY+X'Z
0 0 0	0	0	0	0	0
0 0 1	0	0	1	1	1
0 1 0	0	0	0	0	0
0 1 1	0	1	1	1	1
1 0 0	0	0	0	0	0
1 0 1	0	0	0	0	0
1 1 0	1	0	0	1	1
1 1 1	1	1	0	1	1

2.29 (d)

A B C	A+C	AB+C'	(A+C)(AB+C')	AB	AC'	AB+AC'
0 0 0	0	1	0	0	0	0
0 0 1	1	0	0	0	0	0
0 1 0	0	1	0	0	0	0
0 1 1	1	0	0	0	0	0
1 0 0	1	1	1	0	1	1
1 0 1	1	0	0	0	0	0
1 1 0	1	1	1	1	1	1
1 1 1	1	1	1	1	0	1

2.29 (e)

W X Y Z	W'XY	WZ	W'XY+WZ	W'+Z	W+XY	(W'+Z)(W+XY)
0 0 0 0	0	0	0	1	0	0
0 0 0 1	0	0	0	1	0	0
0 0 1 0	0	0	0	1	0	0
0 0 1 1	0	0	0	1	0	0
0 1 0 0	0	0	0	1	0	0
0 1 0 1	0	0	0	1	0	0
0 1 1 0	1	0	1	1	1	1
0 1 1 1	1	0	1	1	1	1
1 0 0 0	0	0	0	0	1	0
1 0 0 1	0	1	1	1	1	1
1 0 1 0	0	0	0	0	1	0
1 0 1 1	0	1	1	1	1	1
1 1 0 0	0	0	0	0	1	0
1 1 0 1	0	1	1	1	1	1
1 1 1 0	0	0	0	0	1	0
1 1 1 1	0	1	1	1	1	1

2.30

$F = (X+Y')Z + X'YZ'$ (from the circuit)
$= (X+Y'+ X'YZ')(Z+X'YZ')$ (Distributive Law)
$= (X+Y'+X')(X+Y'+Y)(X+Y'+Z')(Z+X')(Z+Y)(Z+Z')$ (Distributive Law)
$= (1+Y')(X+1)(X+Y'+Z')(Z+X')(Z+Y)(1)$ (Complementation Laws)
$= (1)(1)(X+Y'+Z')(Z+X')(Z+Y)(1)$ (Operations with 0 and 1)
$= (X+Y'+Z')(Z+X')(Z+Y)$ (Operations with 0 and 1)

$G = (X +Y' + Z')(X' + Z)(Y + Z)$ (from the circuit)

© 2021 Cengage. All Rights Reserved. May not be scanned, copied or duplicated, or posted to a publicly accessible website, in whole or in part.

Fundamentals of Logic Design Enhanced Edition 7th edition Roth Solutions Manual

© 2021 Cengage. All Rights Reserved. May not be scanned, copied or duplicated, or posted to a publicly accessible website, in whole or in part.

Fundamentals of Logic Design Enhanced Edition 7th edition Roth Solutions Manual